 


Day 4 (Jan 29th)


Sunday, February 2, 2020 2:11 AM

SR Latch



S	R		Q_a	Q_b
0	0		No Change	No Change
0	1		0	1
1	0		1	0
1	1		Prevent This	Prevent This

D Latch

 



E Stands For Enable
D Stands For Data

E	D		Q_a	Q_b
0	X		NC	NC
1	0		0	1
1	1		1	0

Clock Cycle Negative Edge




Negative Edge Triggered D Flip-Flop

  

8 Of these together forms an 8 bit register

Sequential 2s Complementor

 

Input / Output




Q_t	X		Q_{t+1}	Y
0	0		0	0
0	1		1	1
1	0		1	1
1	1		1	0

Q_{t+1} : $Q_t + x$

Y: $Q_t \oplus x$

\oplus means exclusive or

→ 0 → 1

 


D Flip-Flop

X	Q
0	0
1	1

T Flip-Flop

X	Q
0	No Change
1	Complement

Q_t	X		Q_{t+1}
0	0		0
0	1		1
1	0		1
1	1		0

 

			D Flip-	Flop		T Flip-Flop
Q_t	X		Q_{t+1}	Y		I_T
0	0		0	0		0
0	1		1	1		1
1	0		1	1		0
1	1		1	0		0

Going back to the 2s Complementor, it was simpler to use the D flip flop version than the T Version

